





IoT 4211: Sensor Technology

SIGNAL CONDITIONING Part 2

SIGNAL CONDITIONING Part 2



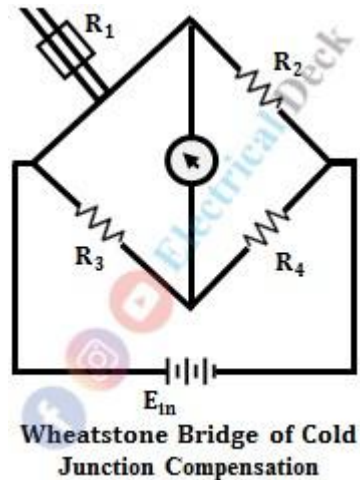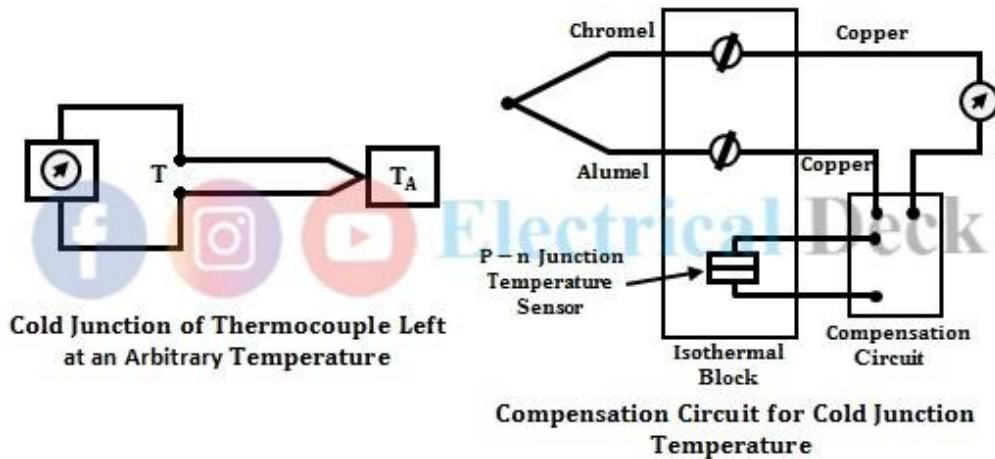Cold Junction Compensation Circuit for Thermocouple



When the measurement circuit consists of a temperature-sensitive compensating resistor then the arrangement is used for cold junction compensation.

The change in ambient temperature affects both the reference junction of a thermocouple and compensating resistor since a temperature-sensitive compensating resistor is placed near the reference junction.

As the temperature of the reference junction increases, the resistance of a temperature-sensitive compensating resistor increases, hence we find some amount of drop in the output emf of the thermocouple. Therefore, the increase in the resistance value of compensating resistor results in a decrease in emf of the thermocouple.

The resistance of the compensating resistor increases with temperature because it is made of a temperature-sensitive material, typically one with a positive temperature coefficient of resistance (PTC). This means that the material's resistance increases as its temperature rises. Here's how it works:


RC Low Pass Filter

cutoff frequency

$$f_L = \frac{1}{2\pi RC}$$

$$V_{out} = V_{in} \times \frac{R_2}{R_1 + R_2} \quad ?$$

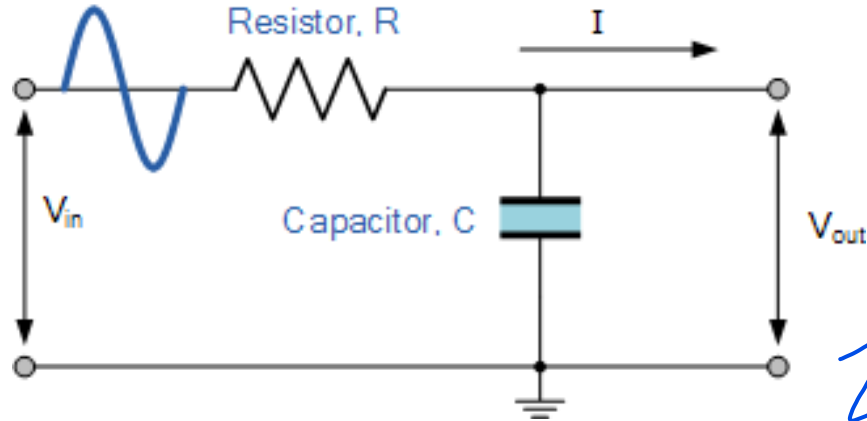
where: $R_1 + R_2 = R_T$, the total resistance of the circuit



We also know that the capacitive reactance of a capacitor in an AC circuit is given as:

$$Z_C = \frac{1}{j\omega C} \quad X_C = \frac{1}{2\pi f C} \text{ in Ohm's}$$

$$\omega = 2\pi f$$

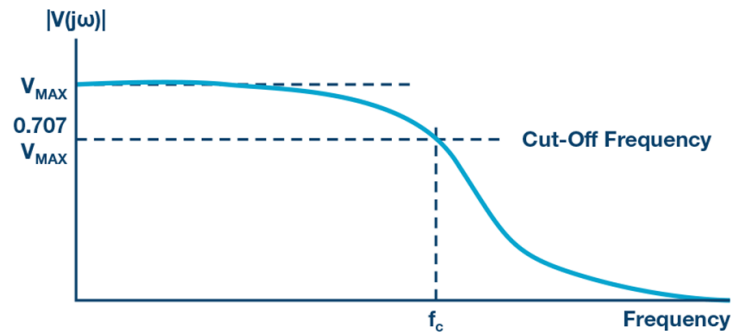

Opposition to current flow in an AC circuit is called **impedance**, symbol Z and for a series circuit consisting of a single resistor in series with a single capacitor, the circuit impedance is calculated as:

$$Z = \sqrt{R^2 + X_C^2}$$

RC Potential Divider Equation

Below the cutoff frequency, the filter passes signals with little attenuation. Above the cutoff frequency, the filter attenuates signals, with the attenuation increasing as the frequency increases.

$$V_{out} = V_{in} \times \frac{X_C}{\sqrt{R^2 + X_C^2}} = V_{in} \frac{X_C}{Z}$$

RC Low Pass Filter

A Low Pass Filter circuit consisting of a resistor of $4k7\Omega$ in series with a capacitor of $47nF$ is connected across a $10v$ sinusoidal supply. Calculate the output voltage at a frequency of $100Hz$.

R

V_{in}



V_{OUT} +

Voltage Output at a Frequency of $100Hz$.

$$X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 100 \times 47 \times 10^{-9}} = 33,863\Omega$$

$$V_{OUT} = V_{IN} \times \frac{X_c}{\sqrt{R^2 + X_c^2}} = 10 \times \frac{33863}{\sqrt{4700^2 + 33863^2}} = 9.9v$$

RC High Pass Filter

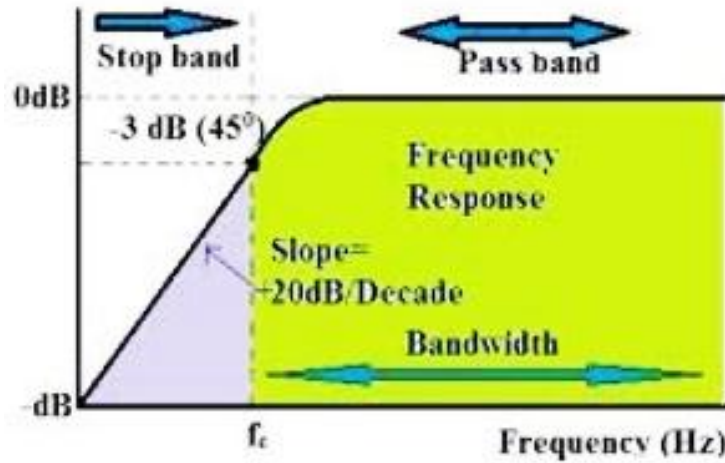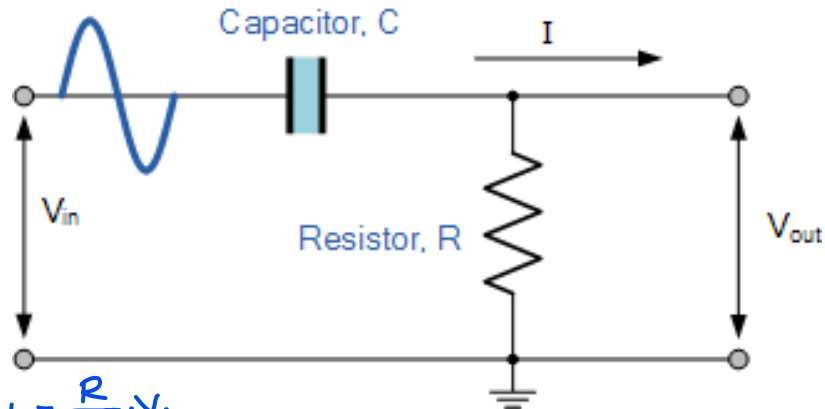

$$V_{out} = \frac{R}{R + X_c} \cdot V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{j\omega C}}$$

$$\Rightarrow H(\omega) = \left| \frac{V_{out}}{V_{in}} \right| = \frac{R}{\sqrt{R^2 + X_c^2}}$$

$$\Rightarrow \frac{1}{\sqrt{2}} = \frac{R}{\sqrt{R^2 + X_c^2}} = \frac{R}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}}$$

$$\Rightarrow \frac{1}{2} = \frac{R^2 \omega^2 C^2}{R^2 \omega^2 C^2 + 1}$$

$$1 + R^2 \omega^2 C^2 = 2 R^2 \omega^2 C^2$$

$$\Rightarrow 1 - R^2 \omega^2 C^2 = 0$$

$$\Rightarrow \omega^2 = \frac{1}{R^2 C^2}$$

$$\Rightarrow \omega = \frac{1}{RC}$$

$$\omega_c = \frac{1}{RC}$$

$$2\pi f_c = \frac{1}{RC}$$

$$f_c = \frac{1}{2\pi RC}$$



$$\phi = \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

$$\omega = 0, \phi = 90^\circ$$

$$\omega = \omega_c, \phi = 45^\circ$$

$$\omega = \infty, \phi = 0^\circ$$

RC Band Pass Filter

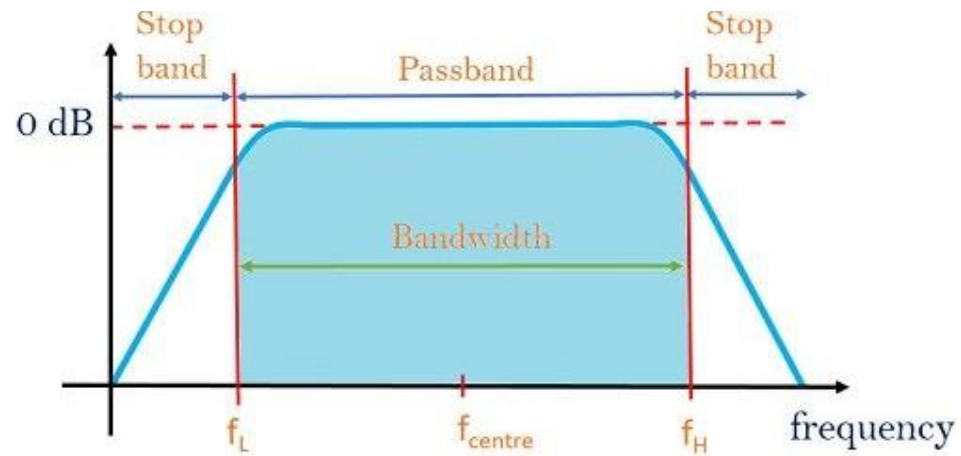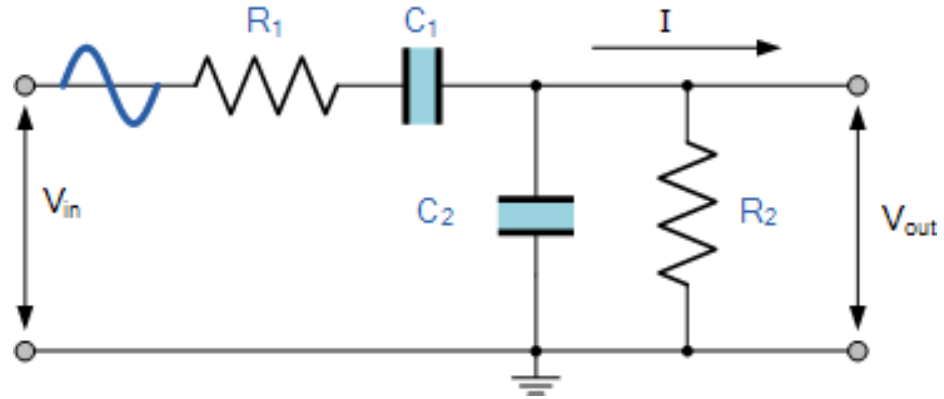

Frequency response curve of a bandpass filter